



VIT

Vellore Institute of Technology

(Deemed to be University under section 3 of UGC Act, 1956)

Continuous Assessment Test I – March 2024

Programme	: B. Tech (ECE/ECM)	Semester	: WS 2023-24
Course	: VLSI System Design	Code	: BECE303L
		Class Nbr.	: CH2023240501057
Faculty	: Dr. Manikandan.P	Slot	: F2+TF2
Time	: 90 Minutes	Max. Marks	: 50

Answer ALL the questions (5*10=50)

Assume and justify if any data is missing.

Q.No.	Sub. Sec.	Questions	Marks
1.		<p>Sketch a color-coded stick diagram for the circuit that implements the Boolean function below;</p> $F = [(XYZ + P(Q + R))]$ <p>Use Euler's methods organize the layout so that the transistors can be implemented on a continuous strip of active.</p>	10
2.		<p>Consider the circuit illustrated in Fig.1. Calculate the propagation delay τ_{pd} at the output node Y for $R = 0$ and ∞. Assume $\left(\frac{W}{L}\right)_1 = \frac{4 \mu m}{1 \mu m}$, $\left(\frac{W}{L}\right)_{2-3} = \frac{1 \mu m}{1 \mu m}$, $C = 10 \text{ pF}$, $\mu_n C_{ox} = 100 \frac{\mu A}{V^2}$, $\mu_p C_{ox} = 50 \frac{\mu A}{V^2}$, $V_{THN} = 1 \text{ V}$, $V_{THP} = -1 \text{ V}$, $\lambda_N = \lambda_P = 0$, $\gamma_N = \gamma_P = 0$, $V_{DD} = 3 \text{ V}$.</p>	10

Fig. 1

- (i) Determine the minimum delay of the path from A to B in the circuit depicted in Fig. 2. Size the gates (X, Y) in order to achieve this delay using two different load capacitors: $C_L = 25$ (5 Marks).
- (ii) Calculate the ratio of NMOS and PMOS in each stage, considering their (W/L) ratios, for the load capacitances mentioned in (i) (5 Marks).

 


Fig. 2

Implement the Boolean expression using pass transistor logic;

$$Y = \overline{(AB) + (CDE) + F}$$

$$K = X(M + N) + PQ$$

Design a logical circuit featuring three inputs and two outputs that adheres to the following conditions:

- When all inputs are at logic 0, both outputs should also be at logic 0.
- When any single input is at logic 1, at least one of the outputs should be at logic 1.
- When any two inputs are at logic 1, at least one of the outputs should be at logic 1.
- When all inputs are at logic 1, both outputs should be at logic 1.

Identify the type of circuit that meets these requirements and implement it using transmission gates.